

Contents

1	Introduction	3
2	Objectives	3
3	Design	3
3.1	Instruction Set	3
3.1.1	Data Transfer Group	4
3.1.2	Machine Control Group	4
3.1.3	Arithmetic Group	5
3.1.4	Branching Group	5
3.1.5	Logical Group	6
3.2	Timing and State Transition	7
4	Architecture	8
4.1	Control Unit (CU)	8
4.2	Arithmetic Logic Unit (ALU)	8
4.3	Registers	9
4.4	Program Counter (PC) Adder.....	10
4.5	Multiplexer 1 (MUX1).....	10
4.6	Multiplexer 2 (MUX2).....	10
4.7	Program Memory (PMem).....	11
4.8	Data Memory (DMem).....	11
5	Implementation using Verilog	12
5.1	Control Unit (CU).....	12
5.2	Arithmetic Logic Unit (ALU).....	14
5.3	Program Counter (PC) Adder.....	16
5.4	Multiplexer (MUX).....	16
5.5	Program Memory (PMem).....	16
5.6	Data Memory (DMem).....	17
5.7	Microcontroller Master Module.....	17
5.8	Testbench.....	21
6	Verification using Sample Instruction Sets	22
6.1	Sample Test 1.....	22
6.2	Sample Test 2.....	24
7	Motivation	26
8	References	26
9	Project Files	26

1 Introduction

The proposed microcontroller design takes into consideration a very simple instruction set. It is non-pipelined (i.e., processes like decoding, fetching, execution and writing memory are merged into a single unit or a single step), and based on Harvard architecture type memory (i.e., separate memories for program and data instructions). The complexity of the instruction sets is reduced when we design on the concept of RISC (Reduced Instruction Set Computer). These techniques help in reducing the amount of space, cycle time, cost and other parameters which are considered for design implementation.

2 Objectives

- This project aims to design the microcontroller based on RISC architecture using Verilog.
- Design of Arithmetic Logic Unit, Control Unit, Registers, Program memory, MUX, Data memory, and Program Counter adder which are to be included in the microcontroller.
- Implementation of different instructions, and verification by simulation.

3 Design

3.1 Instruction Set

On the basis of their *function*, the instructions can be classified as follows

- **Data Transfer Group:** This group of instructions copies data from a location called source to another location called a destination without modifying the content of source.
- **Arithmetic Group:** The arithmetic instructions add, subtract, increment, or decrement data in registers or memory.
- **Logical Group:** This group performs logical (Boolean) operations on data in registers, memory and on condition flags. The logical AND, OR, and Exclusive OR instructions enable us to set specific bits in the accumulator ON or OFF.
- **Branching Group:** The instructions which allow user to change the control of flow of program execution are called branching instructions.
- **Machine Control Group:** This type of instruction alters the different types of operations executed in the processor.

On the basis of *encoding*, the instructions can be classified as follows

- **Type-M instructions:** One operand is from a Data Memory location and the other operand is Accumulator, the result from the arithmetic or logical operation can be stored into the corresponding Data Memory location, or the Accumulator.

- **Type-I instructions:** One operand is the immediate number encoded in the instruction and the other operand is Accumulator, the result from the operation is stored into the Accumulator.
- **Type-S instructions:** These are special instructions which do not require any operand. (for example, No Operation (NOP))

The following sections discuss the various instructions implemented in the proposed microcontroller design. Some of the notations used are as follows

- “aaaa” denotes the address of Data Memory (4-bit).
- “d” denotes the destination of ALU output for type-M instructions. If d = 0, then the result is written to the memory location of the operand. Else, the result is written to the Accumulator.
- “xxxx.xxxx” denotes the immediate number which is used for ALU and branching instructions.

3.1.1 Data Transfer Group

Instruction	Encoding	Function	Flags Affected
MOVAM	0010_0010_aaaa	Move the value of the accumulator to a memory entry. DMem[aaaa] = Acc	None
MOVMA	0011_0011_aaaa	Move the value of memory entry to the accumulator. Acc = DMem[aaaa]	None
MOVIA	1011 xxxx.xxxx	Move Immediate number to accumulator Acc = xxxxxxxx	None
RSV	1010 xxxx.xxxx	Move the value of accumulator to accumulator. (reserved, do nothing) Acc = Acc	None

3.1.2 Machine Control Group

Instruction	Encoding	Function	Flags Affected
NOP	0000_0000_0000	No operation	None

3.1.3 Arithmetic Group

Instruction	Encoding	Function	Flags Affected
ADD	001d.0000_aaaa	Add a memory entry with the accumulator. For d=1, $Acc = Acc + DMem[aaaa]$	Z, C, S, O
SUBAM	001d.0001_aaaa	Subtract an accumulator with a memory entry. For d=1, $Acc = Acc - DMem[aaaa]$	Z, C, S, O
SUBMA	001d.0111_aaaa	Subtract a memory entry by accumulator. For d=1, $Acc = DMem[aaaa] - Acc$	Z, C, S, O
INCM	0010.1000_aaaa	Increment a memory entry $DMem[aaaa] = DMem[aaaa] + 1$	Z, C, S, O
DECM	0010.1001_aaaa	Decrement a memory entry $DMem[aaaa] = DMem[aaaa] - 1$	Z, C, S, O
ADDI	1000 xxxx.xxxx	Add accumulator with immediate number $Acc = Acc + xxxxxxxx$	Z, C, S, O
SUBAI	1001 xxxx.xxxx	Subtract immediate number from accumulator $Acc = Acc - xxxxxxxx$	Z, C, S, O
SUBIA	1111 xxxx.xxxx	Subtract accumulator from immediate number $Acc = xxxxxxxx - Acc$	Z, C, S, O

3.1.4 Branching Group

Instruction	Encoding	Function	Flags Affected
GOTO	0001 xxxx.xxxx	Unconditional branch	None
JZ	0100 xxxx.xxxx	Jump to the instruction indexed by the immediate number, if Z flag is 1	None
JC	0101 xxxx.xxxx	Jump to the instruction indexed by the immediate number, if C flag is 1	None
JS	0110 xxxx.xxxx	Jump to the instruction indexed by the immediate number, if S flag is 1	None
JO	0111 xxxx.xxxx	Jump to the instruction indexed by the immediate number, if O flag is 1	None

3.1.5 Logical Group

Instruction	Encoding	Function	Flags Affected
ANDM	001d_0100.aaaa	Bitwise AND a memory entry with accumulator. For d=0, $DMem[aaaa] = Dmem[aaaa] \text{ AND } Acc$	Z
ANDI	1100 xxxx.xxxx	Bitwise AND accumulator with immediate number $Acc = Acc \text{ AND } xxxxxxxx$	Z
ORM	001d_0101.aaaa	Bitwise OR a memory entry with accumulator. For d=0, $DMem[aaaa] = Dmem[aaaa] \text{ OR } Acc$	Z
ORI	1101 xxxx.xxxx	Bitwise OR accumulator with immediate number $Acc = Acc \text{ OR } xxxxxxxx$	Z
XORM	001d_0110.aaaa	Bitwise XOR a memory entry with accumulator. For d=0, $DMem[aaaa] = Dmem[aaaa] \text{ XOR } Acc$	Z
XORI	1110 xxxx.xxxx	Bitwise XOR accumulator with immediate number $Acc = Acc \text{ XOR } xxxxxxxx$	Z
SLL	0010_1100.aaaa	Shift a memory entry left, by the number of bits specified by accumulator	Z, C
SRL	0010_1101.aaaa	Shift a memory entry right, logical (fill 0), by the number of bits specified by accumulator	Z, C
SRA	0010_1110.aaaa	Shift a memory entry right, arithmetic (fill original MSB), by the number of bits specified by accumulator	Z, C, S
TWOCOMP	0010_1111.aaaa	Take 2's complement of a memory entry, i.e. 0 subtracted by the memory entry $DMem[aaaa] = -DMem[aaaa]$	Z, C, S, O
CIRCSL	0010_1010.aaaa	Circulative shift left a memory entry, by the number of bits specified by accumulator	None
CIRCSR	0010_1011.aaaa	Circulative shift right a memory entry, by the number of bits specified by accumulator	None

3.2 Timing and State Transition

 


Figure 1: Timing and State Transition

There are 30 instructions in total. Each instruction is 12 bits and needs 3 clock cycles to finish, i.e. FETCH stage, DECODE stage, and EXECUTE stage. Note that it is not pipelined. Together with the initial LOAD state, it can be considered as an FSM of 3 states (technically 4 states). These states are

1. **LOAD** (initial state): The program is loaded to the Program Memory. This takes one clock cycle per instruction. After loading is done, then the content of the Program Counter, Instruction Register, Data Register, Status Register, and Accumulator is cleared.
2. **FETCH** (first clock cycle): The current instruction is fetched from the Program Memory. $IR = PMem[PC]$.
3. **DECODE** (second clock cycle): The instruction is decoded to generate the Control Logic and read Data Memory for the operand. $DR = DMem[IR[3:0]]$.
4. **EXECUTE** (third clock cycle): The instruction is executed, as per the following conditions
 - (a) Non-branch instruction: $PC = PC + 1$
 - (b) Branch instruction: if branch is taken, then $PC = IR[7:0]$, else $PC = PC + 1$
 - (c) ALU instruction: if destination is Accumulator, $Acc = ALU\ Out$, else if the destination is Data Memory, $DMem[IR[3:0]] = ALU\ Out$
 - (d) ALU instruction: $SR = ALU\ Status$

SR: Status Register, PC: Program Counter, IR: Instruction Register, Acc: Accumulator.

4 Architecture

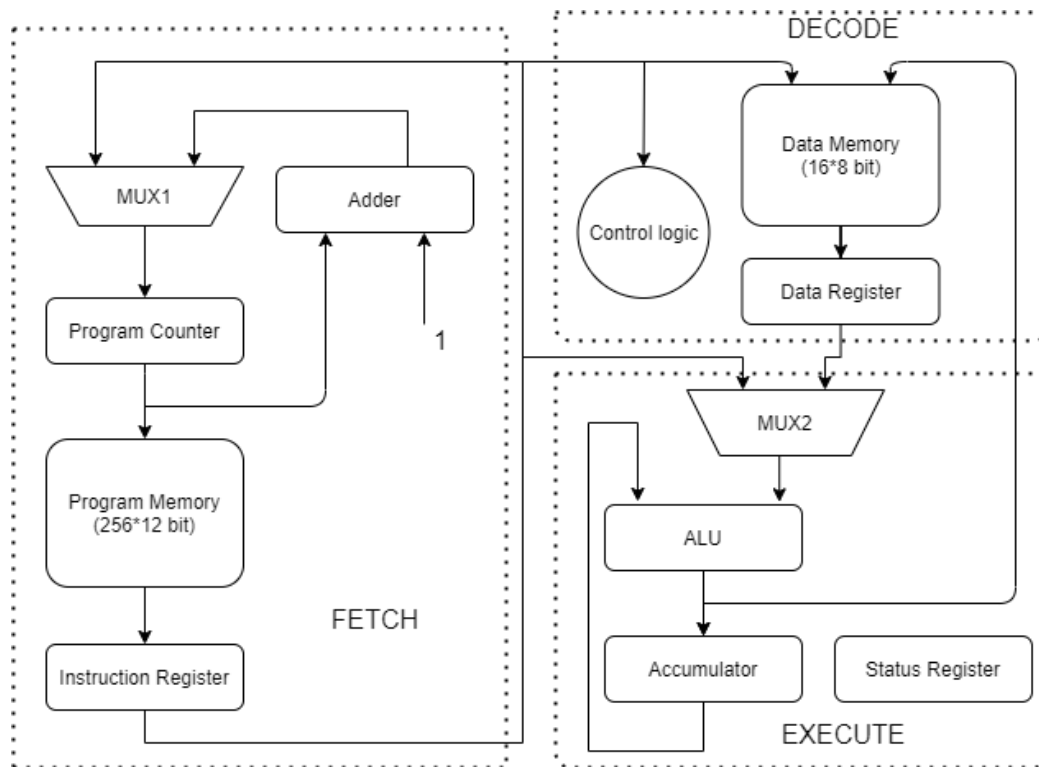


Figure 2: Architecture of the Microcontroller

4.1 Control Unit (CU)

The control signal is determined from the present instruction and present stage. The control logic part consists of only combinational logic components. The 12 control signals provide for the enable signals of PC, Acc, SR, IR, DR, PMem, DMem, ALU, and selection signals for ALU Mode, MUX1 and MUX2. The method to select some of these is listed below.

- In the execution stage
 - (a) *Branching instructions*: Mux1_Sel = SR[IR[9:8]]
 - (b) *ALU type-I instructions*: ALU_Mode = {0, IR[10:8]}.
- PMem_LE is 1 only in Load state else 0.
- The type and category of instruction can be identified by the first four bits (IR[11:8]).

4.2 Arithmetic Logic Unit (ALU)

The Arithmetic Logic Unit (ALU) does the computation for the current instruction. The ALU consists of only combinational logic components. The various ALU ports are listed below.

1. **ALU E** (input, 1-bit, ALU enable port): this port is connected to the Control Logic.

2. **ALU Oper1** (input, 8-bit, ALU operand 1 port): this port is connected to the Accumulator (Acc).
3. **ALU Oper2** (input, 8-bit, ALU operand 2 port): this port is connected to MUX2 Out.
4. **ALU Mode** (input, 4-bit, ALU mode port): this port is connected to the Control Logic.
5. **CFlags** (input, 4-bit, Current flags port): this port is connected to the Status Register (SR).
6. **Flags** (output, 4-bit, ALU flags port): it contains the Zero (Z), Carry (C), Sign (S), Overflow (O) bits, from MSB to LSB, which are connected to the Status Register (SR updated).
7. **ALU Out** (output, 8-bit, ALU output port): connected to the data input port of Data Memory (DI).

4.3 Registers

This microcontroller design has three programmer visible registers. These are as follows

1. **Acc** (8-bit reg, Accumulator): This register holds the result as well as 1 operand of either the arithmetic or the logic calculation.
2. **PC** (8-bit reg, Program Counter): This register stores the index of the instruction which is currently executing.
3. **SR** (4-bit reg, Status Register): This register holds 4 status bits, i.e. Z, C, S, O. Status registers are updated according to operations of the ALU and the accumulator.
 - (a) **SR[3]** (zero flag, Z): it is equal to 1 if the result is zero, otherwise 0.
 - (b) **SR[2]** (carry flag, C): it is equal to 1 if carry is generated, otherwise 0.
 - (c) **SR[1]** (sign flag, S): it is equal to 1 if the result is negative (in 2's complement form), otherwise 0.
 - (d) **SR[0]** (overflow flag, O): it is equal to 1 if the result generates overflow, otherwise 0.

The microcontroller also has two programmer invisible registers (i.e. the programmer cannot manipulate them). They are

1. **DR** (8-bit reg, Data Register): This register stores the operand which is read from the data memory.
2. **IR** (12-bit reg, Instruction Register): This register stores the instruction which is currently executing.

Each one of these registers has an enable port, to specify if the value of the register should be updated in the state transition or not. They are denoted by Acc E, PC E, SR E, DR E, and IR E.

4.4 Program Counter (PC) Adder

PC Adder is used to increment the Program Counter (PC) by 1, i.e. move over to the next instruction. The Adder consists of only combinational logic components. The various ports are listed below.

1. **Adder In** (input, 8-bit, Adder input port): This port is connected to the Program Counter (PC).
2. **Adder Out** (output, 8-bit, Adder output port): This port is connected to the second input port of MUX1 (MUX1_In2).

4.5 Multiplexer 1 (MUX1)

MUX1 is used to select the source for which would update the Program Counter (PC). If the current instruction is not a branch or the branch is not taken, then PC is incremented by 1, else PC is set to the jumping location, IR [7:0]. The various ports are listed below.

1. **MUX1 Sel** (input, 1-bit, MUX1 selection port): this port is connected to the Control Logic.
2. **MUX In1** (input, 8-bit, MUX1 input 1 port): this port is connected to a part of the Instruction Register (IR [7:0]).
3. **MUX In2** (input, 8-bit, MUX1 input 2 port): this port is connected to the output of PC Adder (Adder_Out).
4. **MUX1 Out** (output, 8-bit, MUX1 output port): this port is connected to the Program Counter (PC).

4.6 Multiplexer 2 (MUX2)

MUX2 is used to select the source from which operand 2 of ALU (ALU_Oper2) comes from. If the current executing instruction is of type M, then operand 2 is equal to the Data Register (DR), else if the currently executing instruction is of type I, then operand 2 is equal to a part of Instruction Register (IR [7:0]). The various ports are listed below.

1. **MUX2 Sel** (input, 1-bit, MUX2 selection port): this port is connected to the Control Logic.
2. **MUX2 In1** (input, 8-bit, MUX2 input 1 port): this port is connected to a part of the Instruction Register (IR [7:0]).
3. **MUX2 In2** (input, 8-bit, MUX2 input 2 port): this port is connected to the Data Register (DR).
4. **MUX2 Out** (output, 8-bit, MUX2 output port): this port is connected to operand 2 of the ALU (ALU_Oper2).

4.7 Program Memory (PMem)

This microcontroller design has a Program Memory (PMem) with 256 memory locations which are used to store the program instructions. Each location is 12 bits wide. The input/output ports of the Program memory are listed below.

1. **PMem E** (input, 1-bit, Enable port): If it is 1, then the instruction stored in the memory location indexed by the address port will be readout. If it's 0 then nothing is readout.
2. **PMem Addr** (input, 8-bit, Address port): It specifies the address of the memory location to be readout. It is connected to the Program Counter (PC).
3. **PMem I** (output, 12-bit, Instruction port): The instruction from the location specified by the address port is taken out here. It is connected to the Instruction Register (IR).

There are 3 special ports that are used to load the program (instruction sets) to the program memory in the initial stage of LOADING. They are not used for executing instructions.

1. **PMem LE** (input, 1-bit, Load enable port): if it is 1, then the value of the load instruction input port (load instr) will be stored in the entry corresponding to the address port, else the entry corresponding to the address port will be read out on the Instruction Port (IR updated).
2. **PMem LA** (input, 8-bit, Load address port): Specifies the address of the program memory to be loaded with the instruction.
3. **PMem LI** (input, 12-bit, Load instruction port): Specifies the instruction to be loaded in the program memory in the address specified by the load address port (load addr).

4.8 Data Memory (DMem)

This microcontroller design has a Data Memory (DMem) with 16 memory locations. Each location is 8 bits wide. The various ports for the Data Memory are listed below.

1. **DMem Addr** (input, 4-bit, Address port): Specifies the address of the data memory element to be readout. It is connected to IR[3:0].
2. **DMem E** (input, 1-bit, Enable port): Only if it is 1, then the entry corresponding to the address port will be read out or written in the Data Memory (DR updated).
3. **DMem WE** (input, 1-bit, Write enable port): If it is 1, then the data specified in the data input port is written on to the address corresponding to the address port. Else, the data output port will provide the output from the data memory location corresponding to the address port, whilst ignoring the data in the data input port (DI).
4. **DMem DI** (input, 8-bit, Data input port): It provides the data to be written in the address provided in the address port when the writing operation is enabled. This port is connected to the ALU Out port.
5. **DMem DO** (output, 8-bit, Data output port): The data from the address provided by the address port is read out in this port. this port is connected to MUX2 In1.

5 Implementation using Verilog

5.1 Control Unit (CU)

```

1 module ControlUnit
2   (
3     input [1:0] stage ,           // Load or Fetch or Decode or Execute
4     input [11:0] IR ,            // Instruction Register
5     input [3:0] SR,              // Status Register
6     output reg PC_E , Acc_E , SR_E , IR_E , DR_E , PMem_E ,    // Enable signals
7     output reg PMem_LE , DMem_E , DMem_WE , ALU_E , MUX1_Sel , MUX2_Sel ,
8     output reg [3:0] ALU_Mode    // ALU Output Mode
9   );
10
11 parameter LOAD = 2'b00, FETCH = 2'b01, DECODE = 2'b10, EXECUTE = 2'b11;
12
13 always @(*)
14 begin
15   // Set all enable signals initially to "zero"
16   PMem_LE = 0;
17   PC_E = 0;
18   Acc_E = 0;
19   SR_E = 0;
20   IR_E = 0;
21   DR_E = 0;
22   PMem_E = 0;
23   DMem_E = 0;
24   DMem_WE = 0;
25   ALU_E = 0;
26   ALU_Mode = 4'd0;
27   MUX1_Sel = 0;
28   MUX2_Sel = 0;
29
30   // Load instructions
31   if(stage == LOAD )
32     begin
33       PMem_LE = 1;
34       PMem_E = 1;
35     end
36
37   // Fetch instructions
38   else if(stage == FETCH )
39     begin
40       IR_E = 1;
41       PMem_E = 1;
42     end
43
44   // Decode instructions
45   else if(stage == DECODE )
46     begin
47       // If IR MSB bits are '001' then enable data registers and data
48       memory
49       if( IR[11:9] == 3'b001 )
50         begin
51           DR_E = 1;

```

```

51         DMem_E = 1;
52     end
53
54     else
55         begin
56             DR_E = 0;
57             DMem_E = 0;
58         end
59     end
60
61     // Execute instructions
62     else if(stage == EXECUTE )
63     begin
64         if( IR [11 ]==1 )           // for ALU type-I instructions
65         begin
66             PC_E = 1;
67             Acc_E = 1;
68             SR_E = 1;
69             ALU_E = 1;
70             ALU_Mode = IR[10:8];
71             MUX1_Sel = 1;
72             MUX2_Sel = 0;
73         end
74
75         else if( IR [10 ]==1 )      // for JZ, JC, JS, JO
76         begin
77             PC_E = 1;
78             MUX1_Sel = SR[ IR [9:8]];
79         end
80
81         else if( IR [9]==1 )        // for type-M instructions
82         begin
83             PC_E = 1;
84             Acc_E = IR [8];
85             SR_E = 1;
86             DMem_E = !IR [8];
87             DMem_WE = !IR [8];
88             ALU_E = 1;
89             ALU_Mode = IR [7:4];
90             MUX1_Sel = 1;
91             MUX2_Sel = 1;
92         end
93
94         else if( IR [8]==0 )        // for No Operation (NOP)
95         begin
96             PC_E = 1;
97             MUX1_Sel = 1;
98         end
99
100        else                          // for GOTO
101        begin
102            PC_E = 1;
103            MUX1_Sel = 0;
104        end
105    end

```

```

106 end
107
108 endmodule

```

5.2 Arithmetic Logic Unit (ALU)

```

1 module ALU(
2     input [7:0] Operand1, Operand2,
3     input E,
4     input [3:0] Mode,
5     input [3:0] CFlags,
6     output [7:0] Out,
7     output [3:0] Flags
8     /* 4 Flag bits are Z (zero),
9        C (carry), S (sign), O (overflow)
10        in order from MSB to LSB */
11 );
12
13 wire Z, S, O;
14 reg CarryOut;
15 reg [7:0] Out_ALU;
16
17 always @(*)
18 begin
19     case ( Mode )
20         // Addition Mode
21         4'b0000: {CarryOut, Out_ALU} = Operand1 + Operand2;
22
23         // Subtraction Mode
24         4'b0001: begin
25             Out_ALU = Operand1 - Operand2;
26             CarryOut = !Out_ALU[7];
27         end
28
29         // Move value of accumulator to a memory
30         4'b0010: Out_ALU = Operand1;
31
32         /* Move value of memory entry to accumulator
33            and moving immediate number to accumulator */
34         4'b0011: Out_ALU = Operand2;
35
36         /* Logic Gate Operations between memory entry and accumulator
37            (bitwise operations) */
38         4'b0100: Out_ALU = Operand1 & Operand2; // AND Gate
39         4'b0101: Out_ALU = Operand1 | Operand2; // OR Gate
40         4'b0110: Out_ALU = Operand1 ^ Operand2; // XOR Gate
41
42         // Subtract Memory entry by accumulator
43         4'b0111: begin
44             Out_ALU = Operand2 - Operand1;
45             CarryOut = !Out_ALU[7];
46         end
47     endcase
48 end

```

```

48 // Increment Memory entry by 1
49 4'b1000: {CarryOut, Out_ALU} = Operand2 + 8'h1;
50
51 // Decrement Memory entry by 1
52 4'b1001: begin
53     Out_ALU = Operand2 - 8'h1;
54     CarryOut = !Out_ALU[7];
55 end
56
57 // Left Shift (Circular)
58 4'b1010: Out_ALU = (Operand2 << Operand1[2:0]) | (Operand2 >>
Operand1[2:0]);
59
60 // Right Shift (Circular)
61 4'b1011: Out_ALU = (Operand2 >> Operand1[2:0]) | (Operand2 <<
Operand1[2:0]);
62
63 // Logical Left Shift
64 4'b1100: Out_ALU = Operand2 << Operand1[2:0];
65
66 // Logical Right Shift
67 4'b1101: Out_ALU = Operand2 >> Operand1[2:0];
68
69 // Arithmetic Shift
70 4'b1110: Out_ALU = Operand2 >>> Operand1[2:0];
71
72 // 2's complement generation
73 4'b1111: begin
74     Out_ALU = 8'h0 - Operand2;
75     CarryOut = !Out_ALU[7];
76 end
77
78 default: Out_ALU = Operand2;
79 endcase
80 end
81
82 // Assigning Flags
83 assign O = Out_ALU[7] ^ Out_ALU[6];
84 assign Z = (Out_ALU == 0) ? 1'b1 : 1'b0;
85 assign S = Out_ALU[7];
86
87 assign Flags = {Z, CarryOut, S, O};
88
89 assign Out = Out_ALU;
90
91 endmodule

```

5.3 Program Counter (PC) Adder

```

1 module Adder(In, Out);
2
3     input [7:0] In;
4     output [7:0] Out;
5
6     assign Out = In + 1;
7
8 endmodule

```

5.4 Multiplexer (MUX)

```

1 module MUX(In1, In2, Sel, Out);
2
3     input [7:0] In1, In2;
4     input Sel;
5     output [7:0] Out;
6
7     assign Out = (Sel == 1) ? In1 : In2;
8     // if Sel = 1, then Out = In1, else Out = In2
9
10 endmodule

```

5.5 Program Memory (PMem)

```

1 module PMem(
2     input clk,           // Clock
3     input E,             // Enable Port
4     input [7:0] Addr,    // Address Port
5     output [11:0] I,     // Instruction Port
6     // 3 special ports are used to load program to the memory
7     input LE,            // Load Enable Port
8     input [7:0] LA,      // Load Address Port
9     input [11:0] LI      // Load Instruction Port
10 );
11
12 reg [11:0] Prog_Mem [255:0] ;
13
14 always @(posedge clk)
15 begin
16     // Load Enable = high => copy instructions into Program Memory Register
17     if( LE == 1)
18         Prog_Mem[LA] <= LI;
19 end
20
21 // Enable = high => program memory address is stored in instruction port,
22 // else store "zero"
23 assign I = (E == 1) ? Prog_Mem[Addr] : 0 ;
24 endmodule

```

5.6 Data Memory (DMem)

```

1 module DMem (clk, E, WE, Addr, DI, DO);
2
3     input clk;                // Clock
4     input E;                  // Enable Port
5     input WE;                 // Write Enable
6     input [3:0] Addr;         // Address Port
7     input [7:0] DI;           // Data In
8     output [7:0] DO;          // Data Out
9     reg [7:0] data_mem [15:0];
10
11     always@(posedge clk) begin
12         // Enable port = Write Enable = high => accept data as input
13         if((E == 1) && (WE == 1))
14             data_mem[Addr] <= DI;
15     end
16
17     // Enable port = high => make data available to output, else data out =
18     // zero
19     assign DO = (E == 1)? data_mem[Addr]:0;
20 endmodule

```

5.7 Microcontroller Master Module

```

1 `include "ControlUnit.v"      // Control Unit
2 `include "ALU.v"              // Arithmetic Logic Unit
3 `include "Adder.v"            // PC Adder
4 `include "MUX.v"              // Multiplexer
5 `include "PMem.v"             // Program Memory (256 x 12 bits)
6 `include "DMem.v"             // Data Memory (16 x 8 bits)
7
8 module MicroController(clk, rst);
9     input clk, rst;
10     parameter LOAD = 2'b00, FETCH = 2'b01, DECODE = 2'b10, EXECUTE = 2'b11;
11     reg [1:0] current_state, next_state;
12     reg [11:0] instr_set [25:0];
13     reg load_done;
14     reg [7:0] load_addr;
15     wire [11:0] load_instr;
16     reg [7:0] PC, DR, Acc;     // Program Counter, Data Register, Accumulator
17     reg [11:0] IR;             // Instruction Register
18     reg [3:0] SR;              // Status Register
19     wire PC_E, Acc_E, SR_E, DR_E, IR_E; // Enable signals
20     reg PC_clr, Acc_clr, SR_clr, DR_clr, IR_clr; // Clear signals
21     wire [7:0] PC_updated, DR_updated;
22     wire [11:0] IR_updated;
23     wire [3:0] SR_updated;
24     wire PMem_E, DMem_E, DMem_WE, ALU_E, PMem_LE, MUX1_Sel, MUX2_Sel;
25     wire [3:0] ALU_Mode;       // ALU Output Mode
26     wire [7:0] Adder_Out;
27     wire [7:0] ALU_Out, ALU_Oper2;

```



```

28
29 // Load instructions into Program Memory
30 initial begin
31     $readmemb ("instr_set.dat", instr_set , 0, 25);
32 end
33
34 // Control logic
35 ControlUnit Control_Unit (.stage (current_state ),
36                             .IR( IR),           // Instruction Register
37                             .SR( SR),           // Status Register
38                             .PC_E ( PC_E ),     // PC Enable
39                             .Acc_E ( Acc_E ),   // Accumulator Enable
40                             .SR_E ( SR_E ),     // SR Enable
41                             .IR_E ( IR_E ),     // IR Enable
42                             .DR_E ( DR_E ),     // DR Enable
43                             .PMem_E ( PMem_E ), // PMem Enable
44                             .DMem_E ( DMem_E ), // DMem Enable
45                             .DMem_WE ( DMem_WE ), // DMem Write Enable
46                             .ALU_E ( ALU_E ),   // ALU Enable
47                             .MUX1_Sel( MUX1_Sel), // MUX1 Selection line
48                             .MUX2_Sel( MUX2_Sel), // MUX2 Selection line
49                             .PMem_LE ( PMem_LE ), // PMem Load Enable
50                             .ALU_Mode ( ALU_Mode )); // ALU Output Mode
51
52 // ALU
53 ALU ALU_unit (.Operand 1(Acc),
54               .Operand 2( ALU_Oper2 ),
55               .E( ALU_E ),
56               .Mode ( ALU_Mode ),
57               .CFlags( SR),           // Current Flags
58               .Out( ALU_Out),
59               .Flags( SR_updated ));  // Updated Flags
60 /* 4 Flag bits are Z (zero),
61    C (carry), S (sign), O (overflow )
62    in order from MSB to LSB */
63
64 // PC Adder
65 Adder PC_Adder (.In(PC),
66                 .Out( Adder_Out));
67
68 // MUX1
69 MUX MUX1_unit (.In1 (Adder_Out),
70               .In2 ( IR [7:0]) ,
71               .Sel( MUX1_Sel),
72               .Out( PC_updated ));
73
74 // MUX2
75 MUX MUX2_unit (.In1 (DR),
76               .In2 ( IR [7:0]) ,
77               .Sel( MUX2_Sel),
78               .Out( ALU_Oper2 ));
79
80 // Program Memory
81 PMem PMem_unit (.clk( clk),
82                 .E( PMem_E ),

```

```

83         .Addr( PC),           // Address port
84         .I( IR_updated ),     // Next instruction
85         // 3 special ports, used to load program to the memory
86         .LE( PMem_LE ),       // Load enable port
87         .LA( load_addr),       // Load address port
88         .LI( load_instr));     // Load instruction port
89
90 // Data Memory
91 DMem DMem_unit (.clk( clk),
92                .E( DMem_E ),
93                .WE( DMem_WE ), // Write enable port
94                .Addr( IR[3:0] ), // Address port
95                .DI( ALU_Out),    // Data input port
96                .DO( DR_updated )); // Data output port
97
98 // LOAD
99 always @(posedge clk) begin
100     if( rst == 1) begin
101         load_addr <= 0;
102         load_done <= 1'b0;
103     end
104     else if( PMem_LE == 1) begin
105         load_addr <= load_addr + 8'd1;
106         if( load_addr == 8'd25) begin // All instructions loaded
107             load_addr <= 8'd0;        // into Program Memory
108             load_done <= 1'b1;
109         end
110     else begin
111         load_done <= 1'b0;
112     end
113 end
114
115 assign load_instr = instr_set[ load_addr ];
116
117 // Changing the Current State
118 always @(posedge clk) begin
119     if( rst == 1)
120         current_state <= LOAD;
121     else
122         current_state <= next_state;
123 end
124
125 // State Transitions
126 always @(*) begin
127     PC_clr = 0;
128     Acc_clr = 0;
129     SR_clr = 0;
130     DR_clr = 0;
131     IR_clr = 0;
132     case (current_state)
133     LOAD: begin
134         if( load_done == 1) begin
135             next_state = FETCH; // LOAD -> FETCH
136             PC_clr = 1;         // Set Clear to 1 for all registers
137         end
138     end
139 end

```

```

138         Acc_clr = 1;
139         SR_clr = 1;
140         DR_clr = 1;
141         IR_clr = 1;
142     end
143     else
144         next_state = LOAD;
145     end
146     FETCH: next_state = DECODE;      // FETCH -> DECODE
147
148     DECODE: next_state = EXECUTE;    // DECODE -> EXECUTE
149
150     EXECUTE: next_state = FETCH;    // EXECUTE -> FETCH
151 endcase
152 end
153
154 // Assigning Program Counter, Accumulator, Status Register
155 always @(posedge clk) begin
156     if(rst == 1) begin
157         PC <= 8'd0;                // Clear all registers
158         Acc <= 8'd0;
159         SR <= 4'd0;
160     end
161     else begin
162         if(PC_E == 1'd1)
163             PC <= PC_updated;    // Update Program Counter
164         else if (PC_clr == 1)
165             PC <= 8'd0;        // Clear Program Counter
166         if(Acc_E == 1'd1)
167             Acc <= ALU_Out;    // Update Accumulator
168         else if (Acc_clr == 1)
169             Acc <= 8'd0;        // Clear Accumulator
170         if(SR_E == 1'd1)
171             SR <= SR_updated;    // Update Status Register
172         else if (SR_clr == 1)
173             SR <= 4'd0;        // Clear Status Register
174     end
175 end
176
177 // Assigning Data Register, Instruction Register
178 always @(posedge clk) begin
179     if(DR_E == 1'd1)
180         DR <= DR_updated;    // Update Data Register
181     else if (DR_clr == 1)
182         DR <= 8'd0;        // Clear Data Register
183     if(IR_E == 1'd1)
184         IR <= IR_updated;    // Next Instruction
185     else if (IR_clr == 1)
186         IR <= 12'd0;        // Clear Instruction Register
187 end
188
189 endmodule




```

5.8 Testbench

```

1 `timescale 1ns/10 ps
2 `include "MicroController.v"
3
4 module MicroController_tb;
5
6     reg clk;           // Positive edge triggered clock
7     reg rst;           // Active high reset
8
9     MicroController UUT(.clk(clk), .rst(rst));
10
11     always #5 clk = ~clk;
12     initial begin
13         $dumpfile (" MicroController_tb .vcd ");
14         $dumpvars (0, MicroController_tb);
15         clk = 0;
16         rst = 1;
17         #20 rst = 0;
18         #980 $finish;
19     end
20
21 endmodule

```

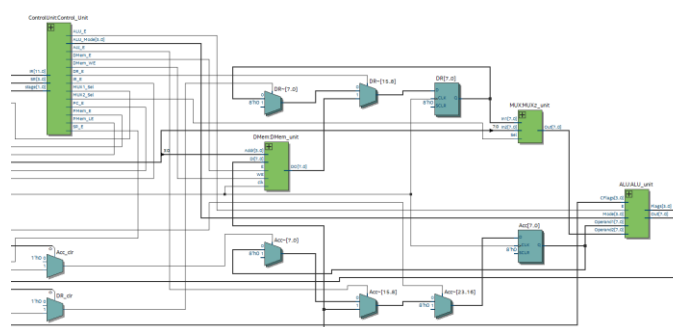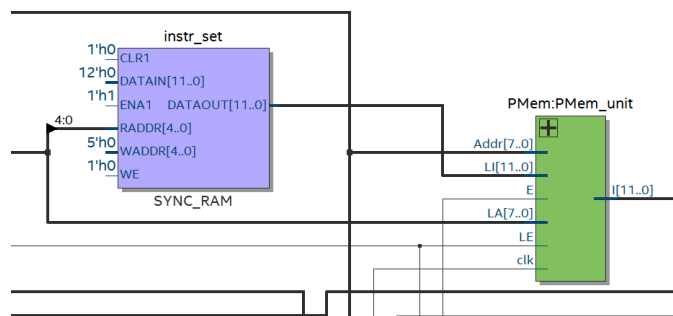 

6 Verification using Sample Instruction Sets

6.1 Sample Test 1

The following instruction set defines the procedure to find out the largest of the three given numbers. Here, we have taken the three numbers as 5, 12, and 2. The complete description of this sample instruction set is given in the table below. From the simulation results, we can observe that the expected output is getting stored in the Accumulator as well as the Data Memory. This instruction set can also be further extended to implement a bubble sorting algorithm.

Instruction Number	Instructions	Encoding	Operation
0	NOP	0000_0000_0000	No Operation
1	MOVIA 0000 0101	1011_0000_0101	Acc = 0000 0101
2	MOVAM 0000	0010_0010_0000	DMem[0] = Acc
3	MOVIA 0000 1100	1011_0000_1100	Acc = 0000 1100
4	MOVAM 0001	0010_0010_0001	DMem[1] = Acc
5	MOVIA 0000 0010	1011_0000_0010	Acc = 0000 0010
6	MOVAM 0010	0010_0010_0010	DMem[2] = Acc
7	SUBMA 0001	0011_0111_0001	Acc = DMem[1] - Acc
8	JS 0001 0000	0110_0001_0000	If s = 1, jump to instruction no 16
9	MOVMA 0001	0011_0011_0001	Acc = DMem[1]
10	SUBMA 0000	0011_0111_0000	Acc = DMem[0] - Acc
11	JS 0000 1110	0110_0000_1110	If s = 1, jump to instruction no 14
12	MOVMA 0000	0011_0011_0000	Acc = DMem[0]
13	GOTO 0001 0110	0001_0001_0110	Go to instruction no 22
14	MOVMA 0001	0011_0011_0001	Acc = DMem[1]
15	GOTO 0001 0110	0001_0001_0110	Go to instruction no 22
16	MOVMA 0010	0011_0011_0010	Acc = DMem[2]
17	SUBMA 0000	0011_0111_0000	Acc = DMem[0] - Acc
18	JS 0001 0101	0110_0001_0101	If s = 1, jump to instruction no 21
19	MOVMA 0000	0011_0011_0000	Acc = DMem[0]
20	GOTO 0001 0110	0001_0001_0110	Go to instruction no 22
21	MOVMA 0010	0011_0011_0010	Acc = DMem[2]
22	MOVAM 0011	0010_0010_0011	DMem[3] = Acc
23	GOTO 0001 0111	0001_0001_0111	Go to instruction no 23

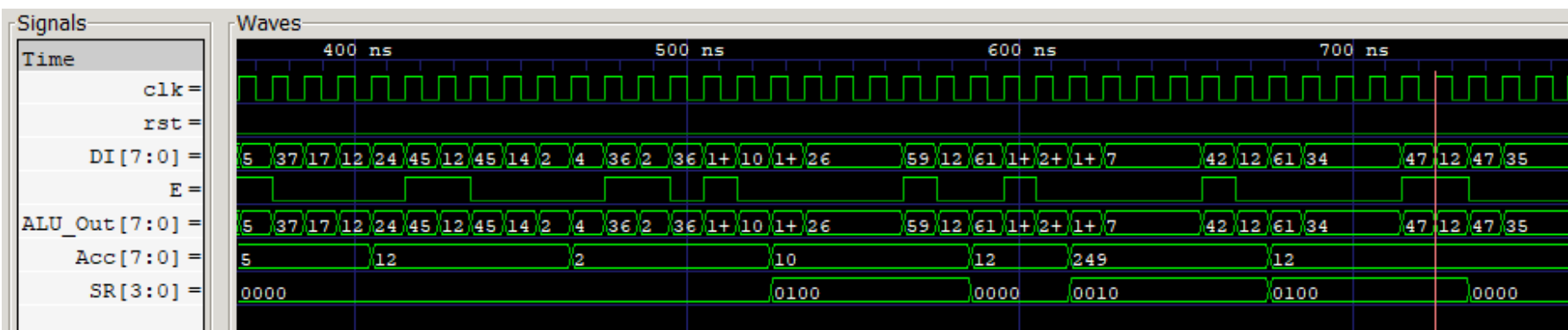


Figure 3: Simulation Results for Sample Test 1

6.2 Sample Test 2

The following instruction set performs both logical and arithmetic operations on the Data Memory and the Accumulator. These operations include, storing a value in the Accumulator, copying the value stored in the Accumulator to a particular memory location and storing the values of desired operations at the specified memory location. The complete description of this sample instruction set is given in the table below. From the simulation results, we can observe that the expected outputs are getting stored at the desired locations.

Instruction Number	Instruction	Encoding	Operation
0	NOP	0000.0000.0000	(no operation)
1	MOVIA Acc, 1	1011.0000.0001	Acc = 1
2	MOVAM DMem[0], Acc	0010.0010.0000	DMem[0] = Acc = 1
3	ADD Acc, Acc, DMem[0]	0011.0000.0000	Acc = Acc + DMem[0] = 1 + 1 = 2
4	ADD DMem[0], Acc, DMem[0]	0010.0000.0000	DMem[0] = Acc + DMem[0] = 1 + 2 = 3
5	SUBAM Acc, Acc, DMem[0]	0011.0001.0000	Acc = Acc - DMem[0] = 2 - 3 = -1
6	SUBAM DMem[0], Acc, DMem[0]	0010.0001.0000	DMem[0] = Acc - DMem[0] = (-1) - 3 = -4
7	SUBMA Acc, DMem[0], Acc	0011.0111.0000	Acc = DMem[0] - Acc = (-4) - (-1) = -3
8	SUBMA DMem[0], DMem[0], Acc	0010.0111.0000	DMem[0] = DMem[0] - Acc = (-4) - (-3) = -1
9	NOP	0000.0000.0000	(no operation)
10	MOVIA Acc, 0x05	1011.0000.0101	Acc = 0x05
11	MOVAM DMem[0], Acc	0010.0010.0000	DMem[0] = Acc = 0x05
12	MOVAM DMem[1], Acc	0010.0010.0001	DMem[1] = Acc = 0x05
13	MOVAM DMem[2], Acc	0010.0010.0010	DMem[2] = Acc = 0x05
14	MOVIA Acc, 0x03	1011.0000.0011	Acc = 0x03
15	ANDM DMem[0], Acc, DMem[0]	0010.0100.0000	DMem[0] = Acc AND DMem[0] = 0x03 AND 0x05 = 0x01
16	ORM DMem[1], Acc, DMem[1]	0010.0101.0001	DMem[1] = Acc OR DMem[1] = 0x03 OR 0x05 = 0x07
17	XORM DMem[2], Acc, DMem[2]	0010.0110.0010	DMem[2] = Acc XOR DMem[2] = 0x03 XOR 0x05 = 0x06
18	GOTO 18	0001.0001.0010	(jump to itself, infinite loop)

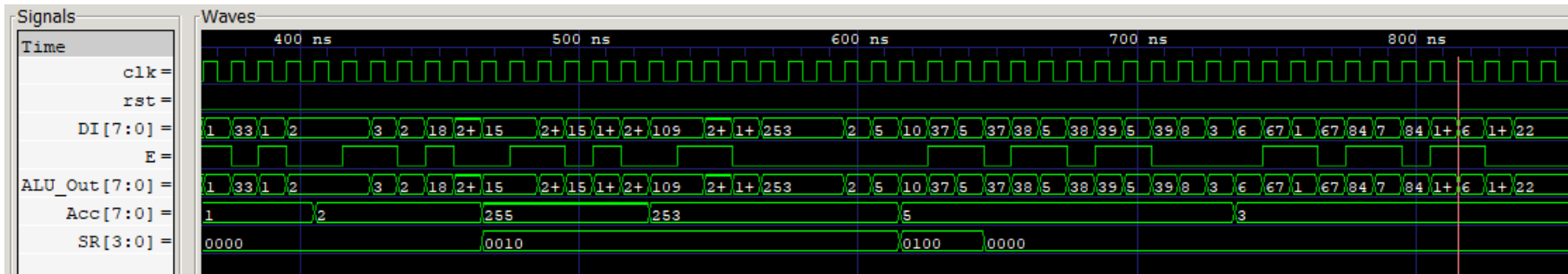


Figure 4: Simulation Results for Sample Test 2

7 Motivation

Electronic devices are being used on a larger basis in day-to-day life and are reaching almost all houses, the most common being mobile phones, laptops, ovens, security systems, and many other devices. All these devices need to be controlled in some way or other. Microcontrollers play a major role in all these control operations. They are very small and flexible. Due to their higher integration, the cost and size of the system are reduced. They are easy to use, and troubleshooting and system maintenance is straightforward. Hence, microcontroller units form a major part of today's society, and their advent has led to many technological advancements.

8 References

1. Aneesh, R., & Jiju, K. (2012, December). Design of FPGA based 8-bit RISC controller IP core using VHDL. In *2012 Annual IEEE India Conference (INDICON)* (pp. 427-432). IEEE. <https://doi.org/10.1109/INDICON.2012.6420656>
2. Gal, R., Golda, A., Frankiewicz, M., & Kos, A. (2011, June). FPGA implementation of 8-bit RISC microcontroller for embedded systems. In *Proceedings of the 18th International Conference Mixed Design of Integrated Circuits and Systems-MIXDES 2011* (pp. 323-328). IEEE.
3. de Pablo, S., Cebrián, J. A., Herrero, L. C., Rey, A. B., & de Antiguones, A. C. (2006). A very simple 8-bit RISC processor for FPGA. In *FPGAworld Conference 2006*.
4. Galani Tina, G., Saini, R., & Daruwala, R. D. (2013). Design and Implementation of 32-bit RISC Processor using Xilinx. *International Journal of Emerging Trends in Electrical and Electronics (IJETEE)*, ISSN, 2320-9569. <https://doi.org/10.5281/zenodo.32433>